

GATE Paper 2010 EE

Electrical Engineering

2010

Q.1 - Q.25 carry one mark each.

1. The value of the quantity P, where $P = \int_0^1 xe^x dx$, is equal to

- (a) 0 (b) 1 (c) e (d) 1/e

(GATE EE 2010)

2. Divergence of the three-dimensional radial vector field \mathbf{r} is

- (a) 3 (b) $1/r$ (c) $\hat{i} + \hat{j} + \hat{k}$ (d) $3(\hat{i} + \hat{j} + \hat{k})$

(GATE EE 2010)

3. The period of the signal $x(t) = 8 \sin\left(0.8\pi t + \frac{\pi}{4}\right)$ is

- (a) 0.4π s (b) 0.8π s (c) 1.25 s (d) 2.5 s

(GATE EE 2010)

4. The system represented by the input-output relationship $y(t) = \int_{-\infty}^{5t} x(\tau) d\tau, t > 0$ is

- (a) Linear and causal (c) Causal but not linear
(b) Linear but not causal (d) Neither linear nor causal

(GATE EE 2010)

5. The switch in the circuit has been closed for a long time. It is opened at $t = 0$. At $t = 0^+$, the current through the $1 \mu\text{F}$ capacitor is

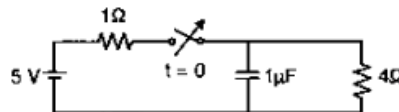


Figure 1

- (a) 0 A (b) 1 A (c) 1.25 A (d) 5 A

(GATE EE 2010)

6. The second harmonic component of the periodic waveform given in the figure has an amplitude of

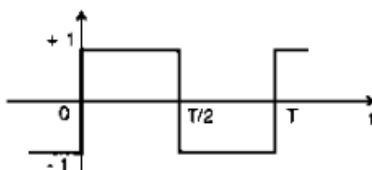


Figure 2

- (a) 0 (b) 1 (c) $2/\pi$ (d) $\sqrt{5}$

(GATE EE 2010)

7. As shown in the figure, a 1Ω resistance is connected across a source that has a load line $v + i = 100$. The current through the resistance is

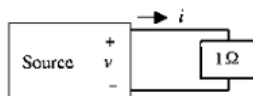


Figure 3

- (a) 25 A (b) 50 A (c) 100 A (d) 200 A

(GATE EE 2010)

8. A wattmeter is connected as shown in the figure. The wattmeter reads

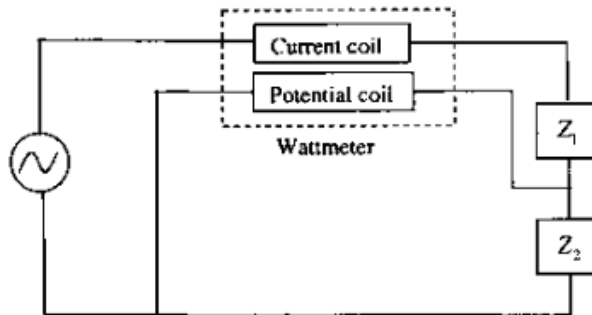


Figure 4

- (a) Zero always
- (b) Total power consumed by Z_1 and Z_2
- (c) Power consumed by Z_1
- (d) Power consumed by Z_2

(GATE EE 2010)

9. An ammeter has a current range of 0-5 A, and its internal resistance is 0.2Ω . In order to change the range to 0-25 A, we need to add a resistance of
- (a) 0.8Ω in series with the meter.
 - (b) 1.0Ω in series with the meter.
 - (c) 0.04Ω in parallel with the meter.
 - (d) 0.05Ω in parallel with the meter.

(GATE EE 2010)

10. As shown in the figure, a negative feedback system has an amplifier of gain 100 with $\pm 10\%$ tolerance in the forward path, and an attenuator of value $9/100$ in the feedback path. The overall system gain is approximately:

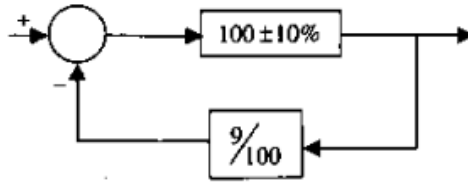


Figure 5

- (a) $10 \pm 1\%$ (c) $10 \pm 5\%$
 (b) $10 \pm 2\%$ (d) $10 \pm 10\%$

(GATE EE 2010)

11. For the system $\frac{2}{(s+1)}$, the approximate time taken for a step response to reach 98% of its final value is

- (a) 1s (b) 2s (c) 4s (d) 8s

(GATE EE 2010)

12. If the electrical circuit of figure (b) is an equivalent of the coupled tank system of figure (a), then

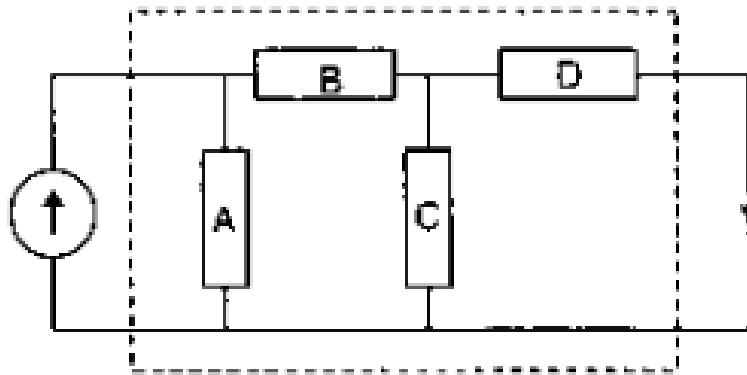


Figure 6

- (a) A, B are resistances and C, D capacitances

- (b) A, C are resistances and B, D capacitances
- (c) A, B are capacitances and C, D resistances
- (d) A, C are capacitances and B, D resistances

(GATE EE 2010)

13. A single-phase transformer has a turns ratio of 1:2, and is connected to a purely resistive load as shown in the figure. The magnetizing current drawn is 1 A, and the secondary current is 1 A. If core losses and leakage reactances are neglected, the primary current is

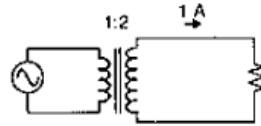


Figure 7

- (a) 1.41 A
- (b) 2 A
- (c) 2.24 A
- (d) 3 A

(GATE EE 2010)

14. Power is transferred from system A to system B by an HVDC link as shown in the figure. If the voltages V_{AB} and V_{CD} are as indicated in the figure, and $i > 0$, then

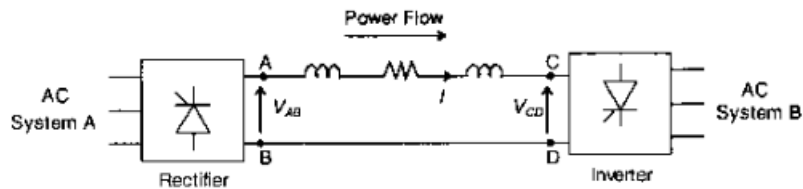


Figure 8

- (a) $V_{AB} < 0$, $V_{CD} < 0$, $V_{AB} > V_{CD}$
- (b) $V_{AB} > 0$, $V_{CD} > 0$, $V_{AB} < V_{CD}$
- (c) $V_{AB} > 0$, $V_{CD} > 0$, $V_{AB} > V_{CD}$

(d) $V_{AB} > 0, V_{CD} < 0$

(GATE EE 2010)

15. A balanced three-phase voltage is applied to a star-connected induction motor, the phase to neutral voltage being V . The stator resistance, rotor resistance referred to the stator, stator leakage reactance, rotor leakage reactance referred to the stator, and the magnetizing reactance are denoted by r_s, r'_r, x_s, x'_r and X_m respectively. The magnitude of the starting current of the motor is given by:

(a) $\frac{V}{\sqrt{(r_s + r'_r)^2 + (x_s + x'_r)^2}}$

(c) $\frac{V}{\sqrt{(r_s + r'_r)^2 + (X_m + x'_r)^2}}$

(b) $\frac{V}{\sqrt{r_s^2 + (x_s + X_m)^2}}$

(d) $\frac{V}{\sqrt{r_s^2 + (X_m + x'_r)^2}}$

(GATE EE 2010)

16. Consider a step voltage wave of magnitude 1 pu travelling along a lossless transmission line that terminates in a reactor. The voltage magnitude across the reactor at the instant the travelling wave reaches the reactor is

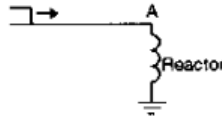


Figure 9

(a) -1 pu

(c) 2 pu

(b) 1 pu

(d) 3 pu

(GATE EE 2010)

17. Consider two buses connected by an impedance of $(0 + j5) \Omega$. The bus 1 voltage is $100 \angle 30^\circ \text{ V}$ and bus 2 voltage is $100 \angle 0^\circ \text{ V}$. The real and reactive power supplied by bus 1, respectively, are

(a) 1000 W, 268 VAR

(c) 276.9 W, -56.7 VAR

(b) -1000 W, -134 VAR

(d) -276.9 W, 56.7 VAR

(GATE EE 2010)

18. A three-phase, 33 kV oil circuit breaker is rated 1200 A, 2000 MVA, 3 s. The symmetrical breaking current is

- (a) 1200 A (c) 35 kA
(b) 3600 A (d) 104.8 kA

(GATE EE 2010)

19. Consider a stator winding of an alternator with an internal high-resistance ground fault. The currents under the fault condition are as shown in the figure. The winding is protected using a differential current scheme with current transformers of ratio 400/5 A as shown. The current through the operating coil is

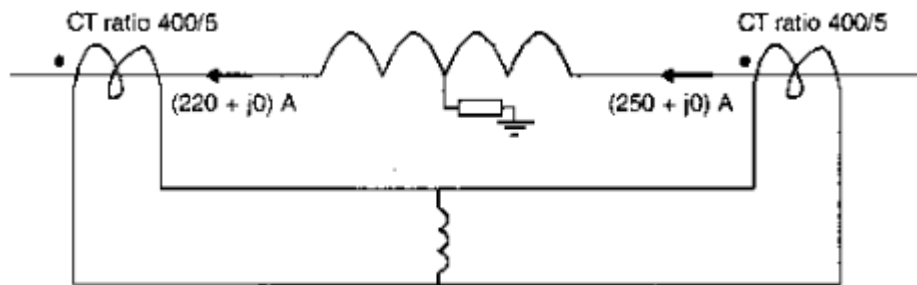


Figure 10

- (a) 0.1875 A (c) 0.375 A
(b) 0.2 A (d) 60 kA

(GATE EE 2010)

20. The zero-sequence circuit of the three phase transformer shown in the figure is

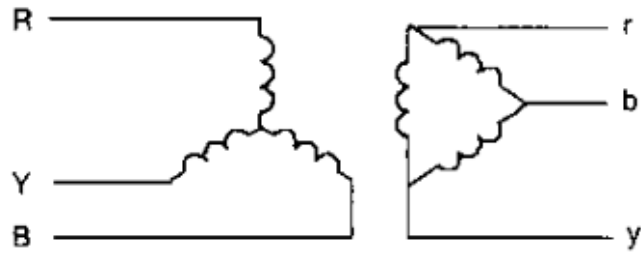


Figure 11

(GATE EE 2010)

21. Given that the op-amp is ideal, the output voltage V_0 is

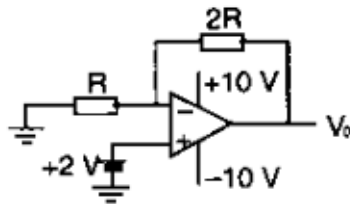


Figure 12

- | | |
|---------|-------------|
| (a) 4 V | (c) 7.5 V |
| (b) 6 V | (d) 12.12 V |

(GATE EE 2010)

22. Assuming that the diodes in the given circuit are ideal, the voltage V_0 is

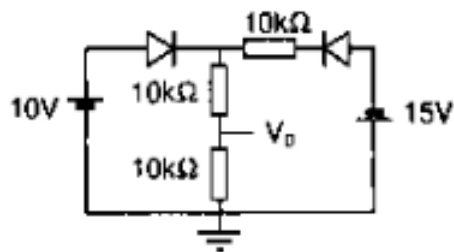


Figure 13

- (a) 4 V
- (b) 5 V
- (c) 7.5 V
- (d) 12.12 V

(GATE EE 2010)

23. The power electronic converter shown in the figure has a single-pole double-throw switch. The pole P of the switch is connected alternately to throws A and B. The converter shown is a

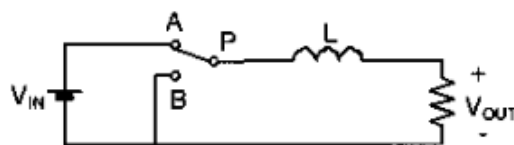


Figure 14

- (a) step-down chopper (*buckconverter*)
- (b) half-wave rectifier
- (c) step-up chopper (*boostconverter*)
- (d) full-wave rectifier

(GATE EE 2010)

24. Figure shows a composite switch consisting of a power transistor (*BJT*) in series with a diode. Assuming that the transistor switch and the diode are ideal, the I-V characteristic of the composite switch is

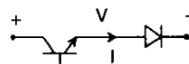


Figure 15: Main Circuit

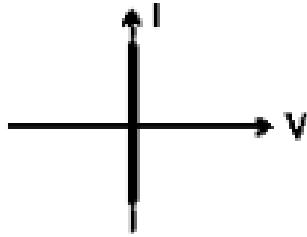


Figure 16: Option A

(a)

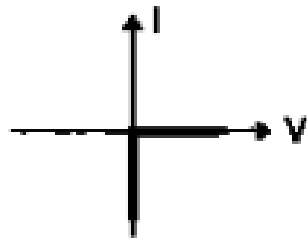


Figure 17: Option B

(b)

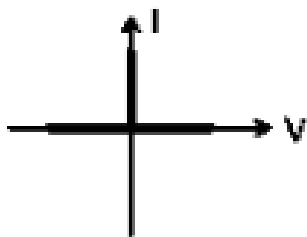


Figure 18: Option C

(c)

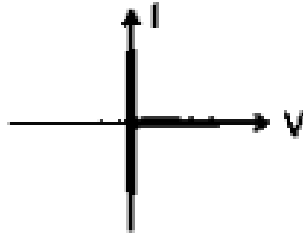


Figure 19: Option D

(d)

(GATE EE 2010)

25. The fully controlled thyristor converter in the figure is fed from a single-phase source. When the firing angle is 0° , the dc output voltage of the converter is 300 V. What will be the output voltage for a firing angle of 60° , assuming continuous conduction?

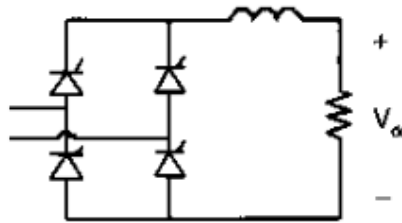


Figure 20

- | | |
|-----------|----------------|
| (a) 150 V | (c) 300 V |
| (b) 210 V | (d) 100π V |

(GATE EE 2010)

Q.26 - Q.55 carry two marks each.

26. At $t = 0$, the function $f(t) = \frac{\sin t}{t}$ has

- (a) a minimum
- (b) a discontinuity
- (c) a point of inflection
- (d) a maximum

(GATE EE 2010)

27. A box contains 4 white balls and 3 red balls. In succession, two balls are randomly selected and removed from the box. Given that the first removed ball is white, the probability that the second removed ball is red is

- (a) $1/3$
- (b) $3/7$
- (c) $1/2$
- (d) $4/7$

(GATE EE 2010)

28. An eigenvector of $P = \begin{pmatrix} 1 & 1 & 0 \\ 0 & 2 & 2 \\ 0 & 0 & 3 \end{pmatrix}$ is

- (a) $[-1 \ 1 \ 1]^T$
- (b) $[1 \ 2 \ 1]^T$
- (c) $[1 \ -1 \ 2]^T$
- (d) $[2 \ 1 \ -1]^T$

(GATE EE 2010)

29. For the differential equation $\frac{d^2x}{dt^2} + 6\frac{dx}{dt} + 8x = 0$ with initial conditions $x(0) = 1$ and $\frac{dx}{dt}|_{t=0} = 0$, the solution is

- (a) $x(t) = 2e^{-4t} - e^{-2t}$
- (b) $x(t) = 2e^{-2t} - e^{-4t}$
- (c) $x(t) = -e^{-6t} + 2e^{-2t}$
- (d) $x(t) = e^{-2t} + 2e^{-4t}$

(GATE EE 2010)

30. For the set of equations, $x_1 + 2x_2 + x_3 + 4x_4 = 2$, $3x_1 + 6x_2 + 3x_3 + 12x_4 = 6$, the following statement is true:

- (a) Only the trivial solution $x_1 = x_2 = x_3 = x_4 = 0$ exists.
- (b) There are no solutions.

- (c) A unique non-trivial solution exists.
- (d) Multiple non-trivial solutions exist.

(GATE EE 2010)

31. $x(t)$ is a positive rectangular pulse from $t = -1$ to $t = +1$ with unit height as shown in the figure. The value of $\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$ where $X(\omega)$ is the Fourier transform of $x(t)$ is

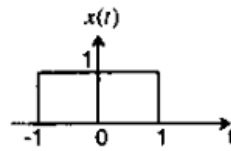


Figure 21

- (a) 2
- (b) 2π
- (c) 4
- (d) 4π

(GATE EE 2010)

32. Given the finite length input $x[n]$ and the corresponding finite length output $y[n]$ of an LTI system as shown below, the impulse response $h[n]$ of the system is

$$x[n] = \{1, -1\} \text{ (arrow at 1)}$$

$$y[n] = \{1, 0, 0, 0, -1\} \text{ (arrow at 1)}$$

- (a) $h[n] = \{1, 0, 0, 1\}$
- (b) $h[n] = \{1, 0, 1\}$
- (c) $h[n] = \{1, 1, 1, 1\}$
- (d) $h[n] = \{1, 1, 1\}$

(GATE EE 2010)

33. If the 12Ω resistor draws a current of 1 A as shown in the figure, the value of resistance R is

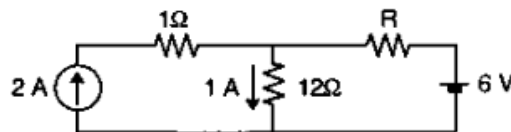


Figure 22

- (a) $4\ \Omega$ (b) $6\ \Omega$ (c) $8\ \Omega$ (d) $18\ \Omega$

(GATE EE 2010)

34. The two-port network P shown in the figure has ports 1 and 2, denoted by terminals (a, b) and (c, d) , respectively. It has an impedance matrix Z with parameters denoted by z_{ij} . A $1\ \Omega$ resistor is connected in series with the network at port 1 as shown in the figure. The impedance matrix of the modified two-port network (shown as a dashed box) is

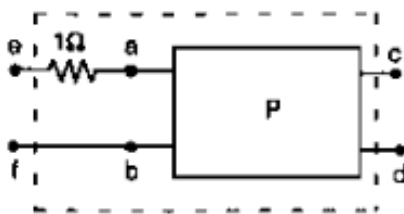


Figure 23

- (a) $\begin{pmatrix} z_{11} + 1 & z_{12} + 1 \\ z_{21} & z_{22} + 1 \end{pmatrix}$ (c) $\begin{pmatrix} z_{11} + 1 & z_{12} \\ z_{21} & z_{22} \end{pmatrix}$
 (b) $\begin{pmatrix} z_{11} + 1 & z_{12} \\ z_{21} & z_{22} + 1 \end{pmatrix}$ (d) $\begin{pmatrix} z_{11} + 1 & z_{12} \\ z_{21} + 1 & z_{22} \end{pmatrix}$

(GATE EE 2010)

35. The Maxwell's bridge shown in the figure is at balance. The parameters of the inductive coil are

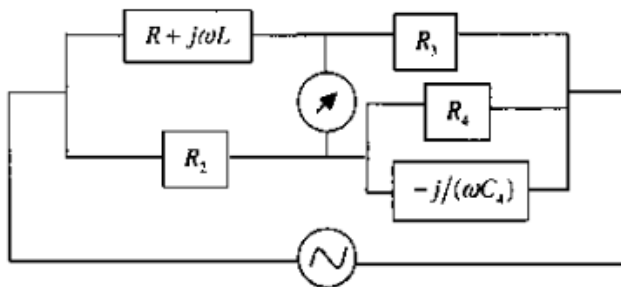


Figure 24

(a) $R = \frac{R_2 R_3}{R_4}, L = C_4 R_2 R_3$

(b) $L = \frac{R_2 R_3}{R_4}, R = C_4 R_2 R_3$

(c) $R = \frac{R_4}{R_2 R_3}, L = \frac{1}{C_4 R_2 R_3}$

(d) $L = \frac{R_4}{R_2 R_3}, R = \frac{1}{C_4 R_2 R_3}$

(GATE EE 2010)

36. The frequency response of $G(s) = 1/[s(s+1)(s+2)]$ plotted in the complex $G(j\omega)$ plane (for $0 \leq \omega < \infty$) is

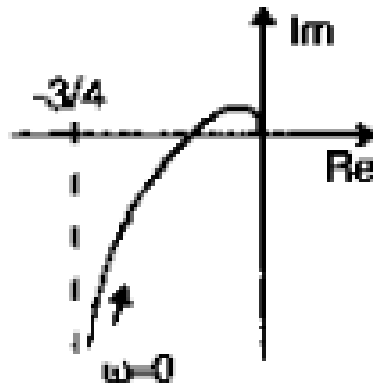


Figure 25

(a)

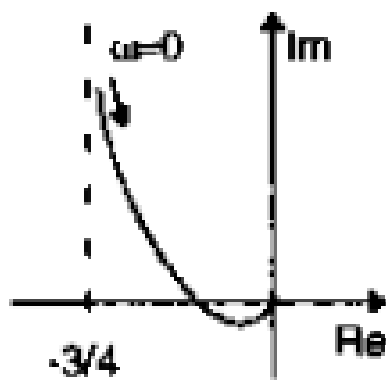


Figure 26

(b)

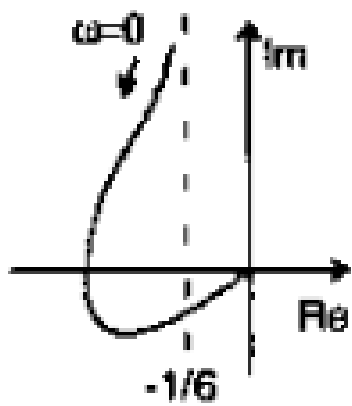


Figure 27

(c)

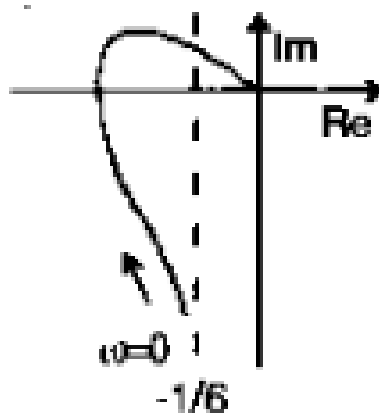


Figure 28

(d)

(GATE EE 2010)

37. The system $\dot{x} = Ax + Bu$ with $A = \begin{pmatrix} -1 & 2 \\ 0 & 2 \end{pmatrix}$, $B = \begin{pmatrix} 0 \\ 1 \end{pmatrix}$ is

- (a) stable and controllable
- (b) stable but uncontrollable
- (c) unstable but controllable
- (d) unstable and uncontrollable

(GATE EE 2010)

38. The characteristic equation of a closed-loop system is $s(s+1)(s+3) + k(s+2) = 0, k > 0$. Which of the following statements is true?

- (a) Its roots are always real
- (b) It cannot have a breakaway point in the range $-1 < \text{Re}[s] < 0$
- (c) Two of its roots tend to infinity along the asymptotes $\text{Re}[s] = -1$
- (d) It may have complex roots in the right half plane.

(GATE EE 2010)

39. A 50 Hz synchronous generator is initially connected to a long lossless transmission line which is open circuited at the receiving end. With the field

voltage held constant, the generator is disconnected from the transmission line. Which of the following may be said about the steady state terminal voltage and field current of the generator?



Figure 29

- (a) The magnitude of terminal voltage decreases, and the field current does not change.
- (b) The magnitude of terminal voltage increases, and the field current does not change.
- (c) The magnitude of terminal voltage increases, and the field current increases.
- (d) The magnitude of terminal voltage does not change, and the field current decreases.

(GATE EE 2010)

40. A separately excited dc machine is coupled to a 50 Hz, three-phase, 4-pole induction machine as shown in the figure. The dc machine is energized first and the machines rotate at 1600 rpm. Subsequently the induction machine is also connected to a 50 Hz, three-phase source, the phase sequence being consistent with the direction of rotation. In steady state,

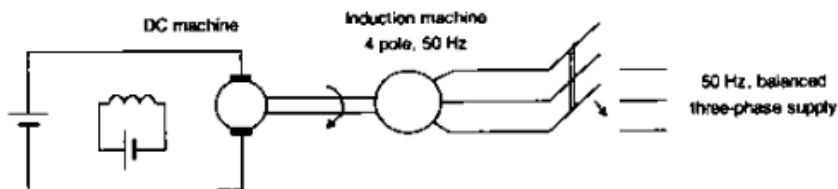


Figure 30

- (a) both machines act as generators
- (b) the dc machine acts as a generator, and the induction machine acts as a motor

- (c) the dc machine acts as a motor, and the induction machine acts as a generator
- (d) both machines act as motors

(GATE EE 2010)

41. A balanced star-connected and purely resistive load is connected at the secondary of a star-delta transformer as shown in the figure. The line-to-line voltage rating of the transformer is 110 V / 220 V. Neglecting the non-idealities of the transformer, the impedance 'Z' of the equivalent star-connected load, referred to the primary side of the transformer, is:

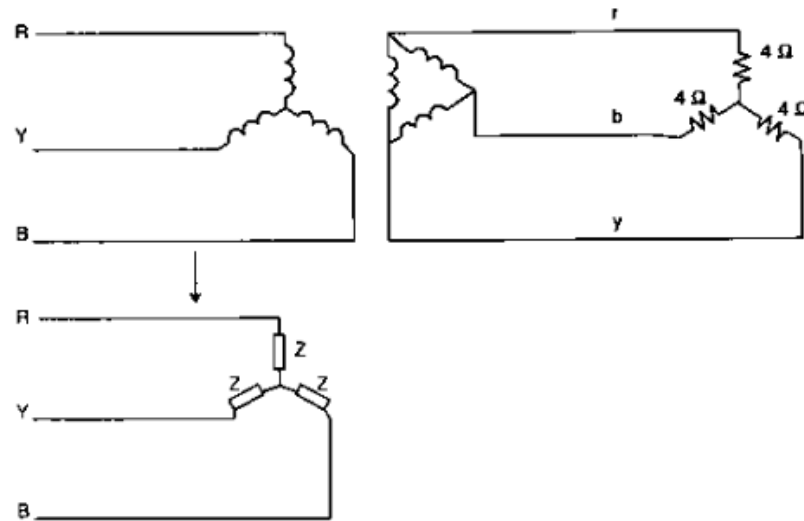


Figure 31

- (a) $(3 + j0)\ \Omega$
- (b) $(0.866 - j0.5)\ \Omega$
- (c) $(0.866 + j0.5)\ \Omega$
- (d) $(1 + j0)\ \Omega$

(GATE EE 2010)

42. Consider a three-phase, 50 Hz, 11 kV distribution system. Each of the conductors is suspended by an insulator string having two identical porcelain insulators. The self capacitance of the insulator is 5 times the shunt capacitance between the link and the ground, as shown in the figure. The voltage across the two insulators are

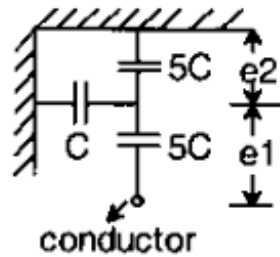


Figure 32

- (a) $e_1=3.74$ kV, $e_2=2.61$ kV (c) $e_1=6.0$ kV, $e_2=4.23$ kV
 (b) $e_1=3.46$ kV, $e_2=2.89$ kV (d) $e_1=5.5$ kV, $e_2=5.5$ kV

(GATE EE 2010)

43. Consider a three-core, three-phase, 50 Hz, 11 kV cable whose conductors are denoted as R, Y and B in the figure. The inter-phase capacitance (C_1) between each pair of conductors is $0.2 \mu\text{F}$ and the capacitance between each line conductor and the sheath is $0.4 \mu\text{F}$. The per-phase charging current is

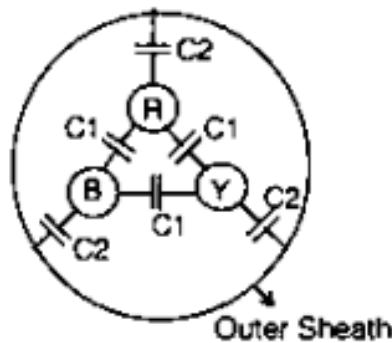


Figure 33

- (a) 2.0 A (b) 2.4 A (c) 2.7 A (d) 3.5 A

(GATE EE 2010)

44. For the power system shown in the figure below, the specifications of the components are the following: G1: 25 kV, 100 MVA, $X = 9\%$ G2: 25 kV,

100 MVA, $X = 9\%$ T1: 25 kV/220 kV, 90 MVA, $X = 12\%$ T2: 220 kV/25 kV, 90 MVA, $X = 12\%$ Line 1: 220 kV, $X=150$ ohms

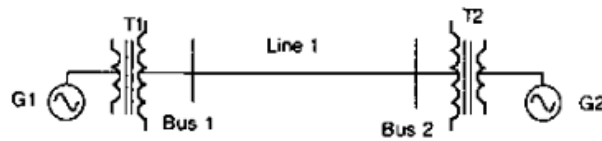


Figure 34

Choose 25 kV as the base voltage at the generator G1, and 200 MVA as the MVA base. The impedance diagram is

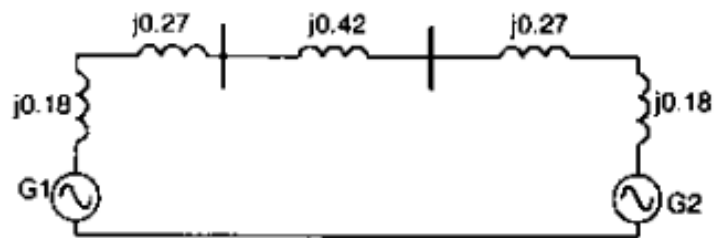


Figure 35

(a)

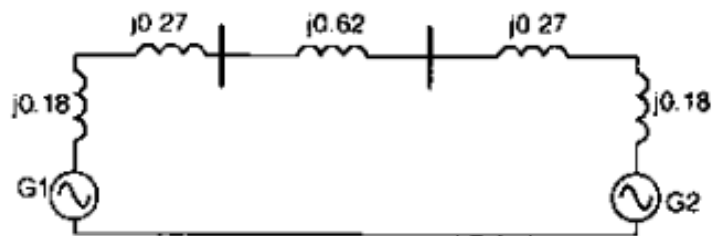


Figure 36

(b)

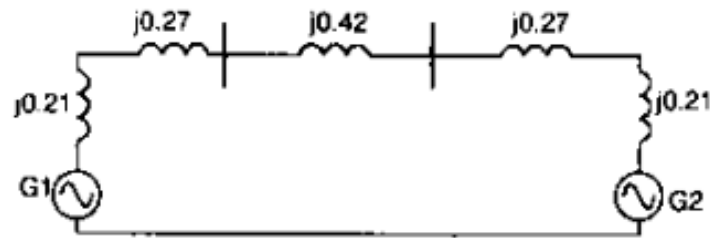


Figure 37

(c)

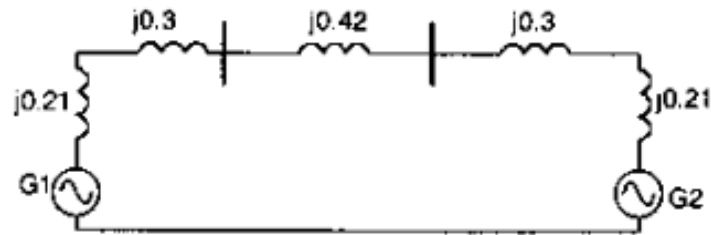


Figure 38

(d)

(GATE EE 2010)

45. The transistor circuit shown uses a silicon transistor with $V_{BE} = 0.7V$, $I_C \approx I_E$ and a dc current gain of 100. The value of V_0 is

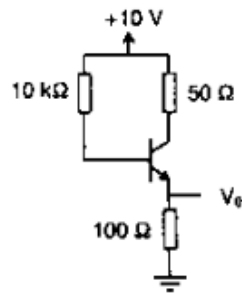


Figure 39

(a) 4.65 V

(c) 6.3 V

(b) 5 V

(d) 7.23 V

(GATE EE 2010)

46. The TTL circuit shown in the figure is fed with the waveform X (*also shown*). All gates have equal propagation delay of 10 ns. The output Y of the circuit is

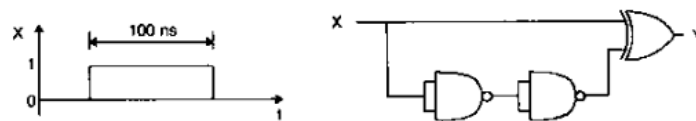


Figure 40

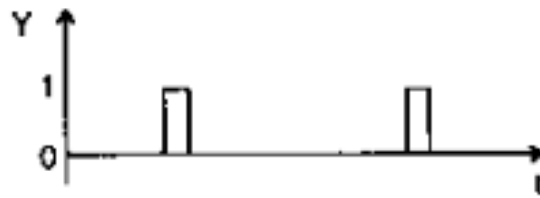


Figure 41

(a)

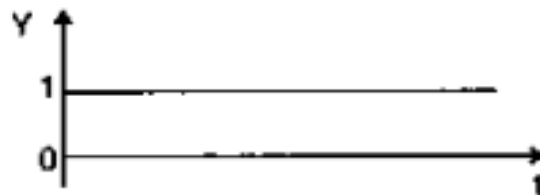


Figure 42

(b)

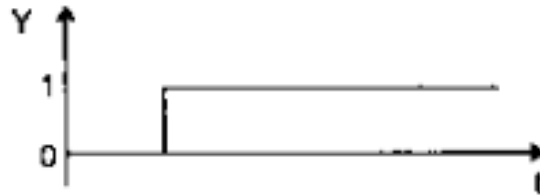


Figure 43

(c)

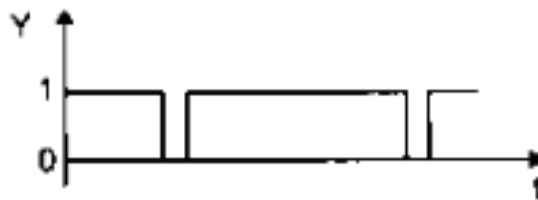


Figure 44

(d)

(GATE EE 2010)

47. When a "CALL Addr" instruction is executed, the CPU carries out the following sequential operations internally: Note: (R) means content of register R, $((R))$ means content of memory location pointed to by R, PC means Program Counter, SP means Stack Pointer

- (a) (SP) incremented; $(PC) \leftarrow Addr$; $((SP)) \leftarrow (PC)$
- (b) $(PC) \leftarrow Addr$; $((SP)) \leftarrow (PC)$; (SP) incremented
- (c) $(PC) \leftarrow Addr$; (SP) incremented; $((SP)) \leftarrow (PC)$
- (d) $((SP)) \leftarrow (PC)$; (SP) incremented; $(PC) \leftarrow Addr$

(GATE EE 2010)

Common Data for Questions 48 and 49:

A separately excited DC motor runs at 1500 rpm under no-load with 200 V applied to the armature. The field voltage is maintained at its rated value. The speed of the motor, when it delivers a torque of 5 Nm, is 1400 rpm as shown in the figure. The rotational losses and armature reaction are neglected.

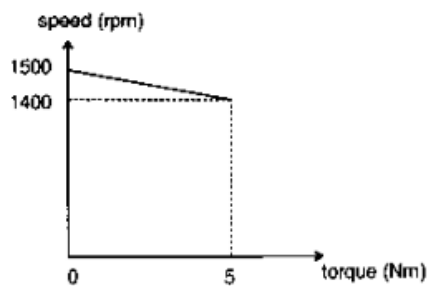


Figure 45

48. The armature resistance of the motor is

- | | |
|------------------|------------------|
| (a) 2Ω | (c) 4.4Ω |
| (b) 3.4Ω | (d) 7.7Ω |

(GATE EE 2010)

49. For the motor to deliver a torque of 2.5 Nm at 1400 rpm, the armature voltage to be applied is

- | | |
|-------------|-------------|
| (a) 125.5 V | (c) 200 V |
| (b) 193.3 V | (d) 241.7 V |

(GATE EE 2010)

Common Data for Questions 50 and 51:

Given $f(t)$ and $g(t)$ as shown below:



Figure 46

50. $g(t)$ can be expressed as

- (a) $g(t) = f(2t - 3)$ (c) $g(t) = f\left(2t - \frac{3}{2}\right)$
 (b) $g(t) = f\left(\frac{t}{2} - 3\right)$ (d) $g(t) = f\left(\frac{t}{2} - \frac{3}{2}\right)$

(GATE EE 2010)

51. The Laplace transform of $g(t)$ is

- (a) $\frac{1}{s} (e^{3s} - e^{5s})$ (c) $\frac{e^{-3s}}{s} (1 - e^{-2s})$
 (b) $\frac{1}{s} (e^{-3s} - e^{-5s})$ (d) $\frac{1}{s} (e^{-5s} - e^{-3s})$

(GATE EE 2010)

Statement for Linked Answer Questions 52 and 53:

The following Karnaugh map represents a function F.

	YZ			
	00	01	11	10
X=0	1	1	1	0
X=1	0	0	1	0

Table 1

52. A minimized form of the function F is

(a) $F = \overline{X}Y + YZ$

(c) $F = \overline{X}\overline{Y} + Y\overline{Z}$

(b) $F = \overline{X}\overline{Y} + YZ$

(d) $F = \overline{X}\overline{Y} + \overline{Y}Z$

(GATE EE 2010)

53. Which of the following circuits is a realization of the above function F?

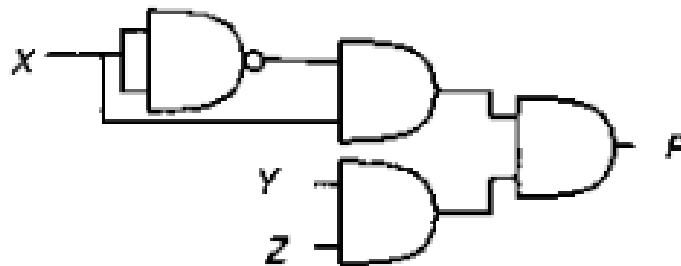


Figure 47

(a)

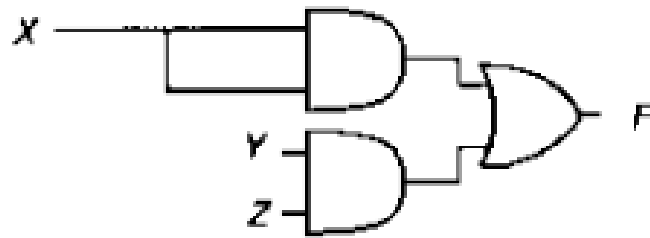


Figure 48

(b)

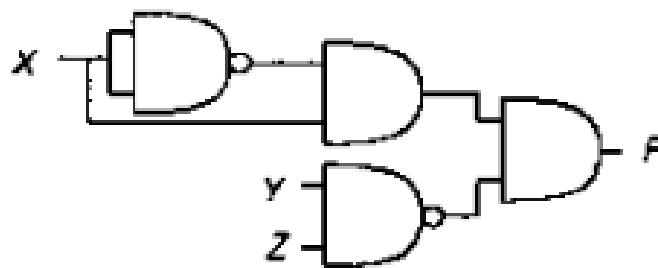


Figure 49

(c)

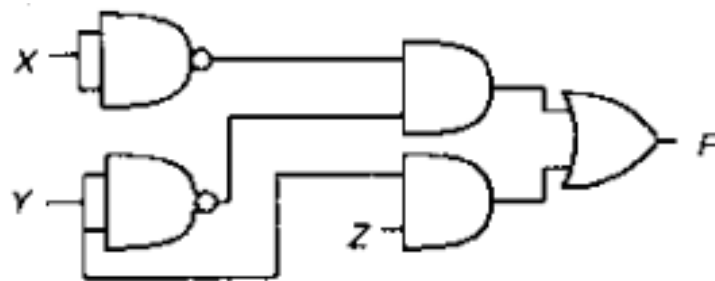


Figure 50

(d)

(GATE EE 2010)

Statement for Linked Answer Questions 54 and 55:

The L-C circuit shown in the figure has an inductance $L = 1 \text{ mH}$ and a capacitance $C = 10 \mu\text{F}$.

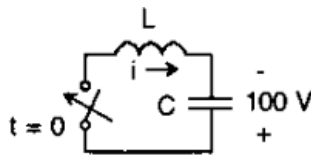


Figure 51

54. The initial current through the inductor is zero, while the initial capacitor voltage is 100 V. The switch is closed at $t = 0$. The current i through the circuit is:

- (a) $5 \cos(5 \times 10^3 t) \text{ A}$ (c) $10 \cos(5 \times 10^3 t) \text{ A}$
(b) $5 \sin(10^4 t) \text{ A}$ (d) $10 \sin(10^4 t) \text{ A}$

(GATE EE 2010)

55. The L-C circuit of Q54 is used to commutate a thyristor, which is initially carrying a current of 5 A as shown in the figure below. The values and initial conditions of L and C are the same as in Q54. The switch is closed at $t = 0$. If the forward drop is negligible, the time taken for the device to turn off is

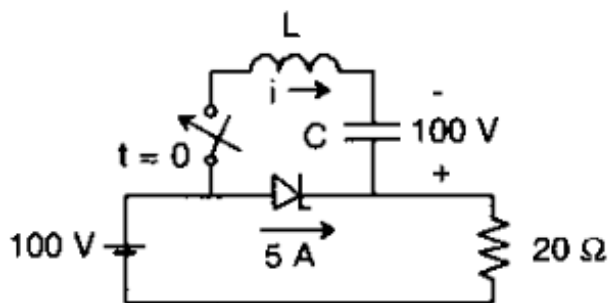


Figure 52

(a) $52\ \mu\text{s}$

(b) $156\ \mu\text{s}$

(c) $312\ \mu\text{s}$

(d) $26\ \mu\text{s}$

(*GATE EE* 2010)

General Aptitude (GA) Questions

Q.56 - Q.60 carry one mark each.

56. 25 persons are in a room. 15 of them play hockey, 17 of them play football and 10 of them play both hockey and football. Then the number of persons playing neither hockey nor football is:

(a) 2 (b) 17 (c) 13 (d) 3

(GATE EE 2010)

57. Choose the most appropriate word from the options given below to complete the following sentence: If we manage to _____ our natural resources, we would leave a better planet for our children.

(a) uphold (c) cherish
(b) restrain (d) conserve

(GATE EE 2010)

58. The question below consists of a pair of related words followed by four pairs of words. Select the pair that best expresses the relation in the original pair. Unemployed: Worker

(a) fallow: land
(b) unaware: sleeper
(c) wit: jester
(d) renovated: house

(GATE EE 2010)

59. Which of the following options is the closest in meaning to the word below: Circuitous

(a) cyclic (c) confusing
(b) indirect (d) crooked

(GATE EE 2010)

60. Choose the most appropriate word from the options given below to complete the following sentence: His rather casual remarks on politics ----- his lack of seriousness about the subject.

(a) masked (c) betrayed
(b) belied (d) suppressed

(GATE EE 2010)

Q.61 - Q.65 carry two marks each.

61. Hari (*H*), Gita (*G*), Irfan (*I*) and Saira (*S*) are siblings (*i.e. brothers and sisters*). All were born on 1st January. The age difference between any two successive siblings (*that is born one after another*) is less than 3 years. Given the following facts:

- i. Hari's age + Gita's age \leq Irfan's age + Saira's age.
- ii. The age difference between Gita and Saira is 1 year. However, Gita is not the oldest and Saira is not the youngest.
- iii. There are no twins.

In what order were they born (*oldest first*)?

(a) HSI G (b) SGHI (c) IGSH (d) IHSG

(GATE EE 2010)

62. 5 skilled workers can build a wall in 20 days; 8 semi-skilled workers can build a wall in 25 days; 10 unskilled workers can build a wall in 30 days. If a team has 2 skilled, 6 semi-skilled and 5 unskilled workers, how long will it take to build the wall?

(a) 20 days (b) 18 days (c) 16 days (d) 15 days

(GATE EE 2010)

63. Modern warfare has changed from large scale clashes of armies to suppression of civilian populations. Chemical agents that do their work silently appear to be suited to such warfare; and regretfully, there exist people in military establishments who think that chemical agents are useful tools for

their cause. Which of the following statements best sums up the meaning of the above passage:

- (a) Modern warfare has resulted in civil strife.
- (b) Chemical agents are useful in modern warfare.
- (c) Use of chemical agents in warfare would be undesirable.
- (d) People in military establishments like to use chemical agents in war.

(GATE EE 2010)

64. Given digits 2, 2, 3, 3, 3, 4, 4, 4, 4 how many distinct 4 digit numbers greater than 3000 can be formed?

- (a) 50
- (b) 51
- (c) 52
- (d) 54

(GATE EE 2010)

65. If $137 + 276 = 435$ how much is $731 + 672$?

- (a) 534
- (b) 1403
- (c) 1623
- (d) 1513

(GATE EE 2010)